



**The University of Azad Jammu & Kashmir, Muzaffarabad**

## **Computer Architecture & Logic Design**

Verification of DE Morgan's Laws

**Student Name:**

Shahzad Ahmed Awan

**Roll No:**

2024-SE-15

**Course Title:**

Computer Architecture & Logic Design

**Course Code:**

CS-1205

**Instructor:**

Engr. Sidra Rafique

**Submission Date:**

03-June -2025

**Department of Software Engineering**

## De Morgan's First Law Verification

$$(A \cdot B)' = A' + B'$$

### Objective:

To verify De Morgan's First Law practically using basic logic gates.

- Used the ICs: **7408 (AND)**, **7404 (NOT)**, and **7432 (OR)**.
- These ICs were inserted on the trainer board.
- VCC and GND connections were made to each IC using the trainer's power rails.
- **Left Side (LHS):** Connected inputs A and B to the **AND gate**, then connected the output of the AND gate to the **NOT gate**. The NOT gate's output was connected to **LED1** to observe  $(A \cdot B)'$ .

 


Figure 1: De morgan Law -1

- **Right Side (RHS):** Connected A and B each to individual **NOT gates**, and connected their outputs to an **OR gate**. The OR gate's output was connected to **LED2** to observe  $A' + B'$ .

- The input switches were toggled through all 4 combinations: 00, 01, 10, and 11.
- In every case, **LED1 and LED2 gave the same output**, proving the law.

### **(A) Gate-Level Circuit**

Circuit built using basic gates (not IC models)

- Opened EWB and created a new project.
- Added two logic switches as inputs **A** and **B**.
- Connected A and B to an **AND gate**, then the output to a **NOT gate**, and connected the output of that to **LED1** — representing  $(A \cdot B)'$ .
- Separately, connected A and B to **two NOT gates**, then their outputs to an **OR gate**, and its output to **LED2** — representing  $A' + B'$ .
- Toggled input switches through all 4 combinations.
- Both LEDs gave identical outputs, confirming correctness.

### **EWB Implementation – De Morgan's First Law**

#### **ICs Used in EWB Simulation:**

- **7408** – AND Gate
- **7404** – NOT Gate (2 ICs)
- **7432** – OR Gate

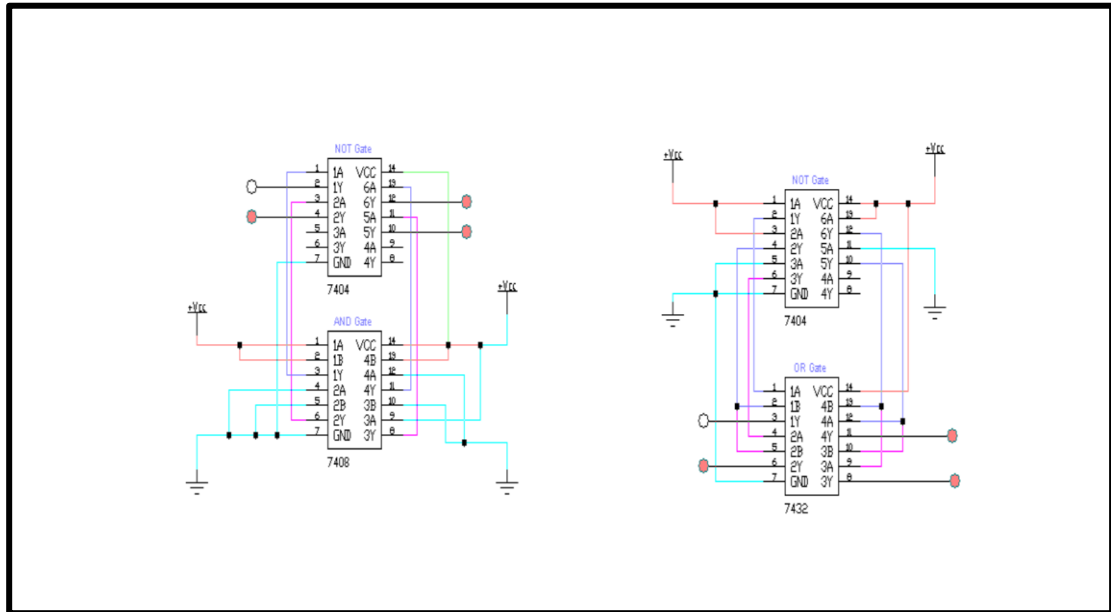


Figure 2: DE Morgan First Law ICs Circuit Verification

### Setup for Left-Hand Side (LHS): $(A \cdot B)'$

1. Placed **7408 AND Gate IC** on the EWB trainer board.
2. Connected input A and B manually by using input logic controls in EWB (no switches used).
3. Connected the output of the AND gate to a **NOT gate (7404)**.
4. Attached four **virtual LEDs** at the output of the NOT gate for all four combinations:
  - $A = 0, B = 0$
  - $A = 0, B = 1$
  - $A = 1, B = 0$
  - $A = 1, B = 1$
5. Powered the ICs with virtual **VCC (+5V)** and **GND** terminals.

### Setup for Right-Hand Side (RHS): $A' + B'$

1. Connected A and B separately to **two NOT gates (7404)** to get  $A'$  and  $B'$ .

2. Fed the inverted outputs into the **7432 OR Gate IC**.
3. Attached **four LEDs** to the output of this OR gate, again for the same four combinations.

### Result Verification:

- The output LEDs of both LHS and RHS circuits were checked side by side.
- **All outputs matched** for each input combination (00, 01, 10, 11).
- This successfully verified **De Morgan's First Law** virtually using ICs in EWB.

### Truth Tables: $(A \cdot B)' = A' + B'$

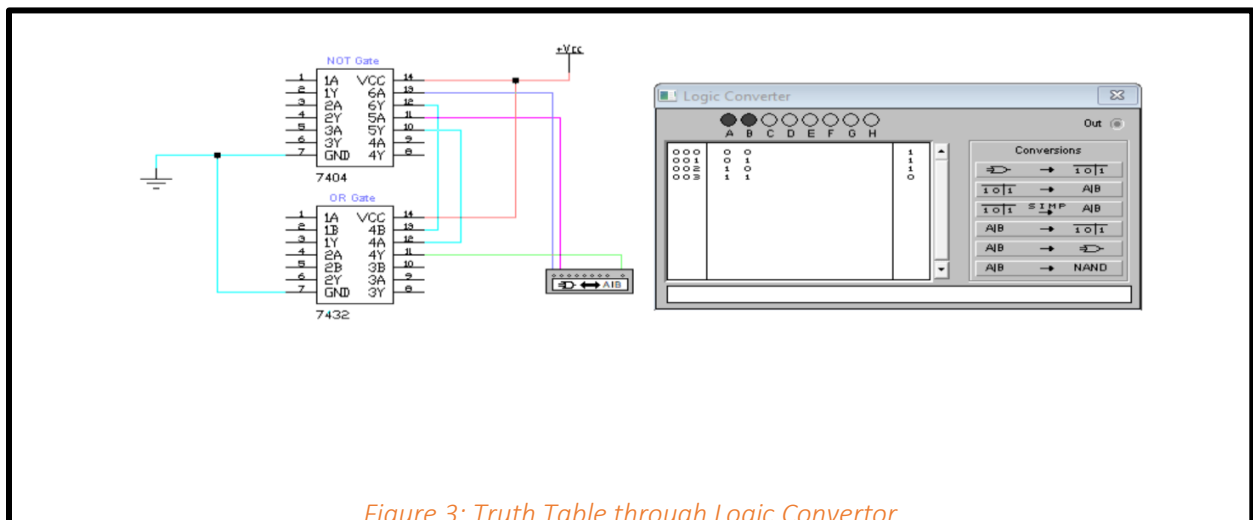


Figure 3: Truth Table through Logic Converter

A	B	$A \cdot B$	$(A \cdot B)'$	$A'$	$B'$	$A' + B'$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

# **De Morgan's Second Law**

$$(A + B)' = A' \cdot B'$$


## **Lab Implementation (Digital Trainer Board – Practical Setup)**

### **Objective:**

To verify De Morgan's Second Law by practically implementing both sides of the expression on the digital trainer board using ICs, power supply, and LEDs.

### **Left-Hand Side (LHS): $(A + B)'$**

 1. Placed the **7432 OR Gate IC** on the digital trainer board.
2. Connected input A and B using wired input lines from the trainer board input section.
3. Output of the OR gate was connected to the **7404 NOT Gate IC** to invert  $(A + B)$ .
4. Four different combinations (00, 01, 10, 11) were tested manually.



5. Output was connected to **LED** to verify the result visually for each case.

### **Right-Hand Side (RHS): $A' \cdot B'$**

1. Inputs A and B were separately connected to **two NOT gates** (using 7404 IC) to get A' and B'.
  2. The outputs of those NOT gates were connected to a **7408 AND Gate IC**.
  3. Four combinations were again applied.
  4. Output of the AND gate was connected to an **LED**.
  5. Outputs from both sides were compared — **both were same for all inputs**, proving the law.
- 

## **EWB Implementation**

The simulation was done in **two ways**:

1. Using GATE-based circuit
  2. Using **IC-based circuit on virtual trainer board** in EWB  
(No switches used, inputs controlled using built-in logic tools of EWB)
- 

## **Gate-Level Circuit Implementation in EWB**

### **LHS: $(A + B)'$**

1. Placed **OR Gate** from the EWB component library.
2. Connected inputs A and B using logic toggles.
3. Output of OR gate was passed through a **NOT gate** to invert the result.
4. LED was attached to output to display the final result.

### **RHS: $A' \cdot B'$**

1. Connected A and B separately to **two NOT gates**.
2. Connected their outputs to an **AND gate**.
3. Final output from AND was connected to another LED.
4. Switched between combinations using toggles and verified both outputs matched.

## IC-Level Circuit Implementation in EWB

### ICs Used:

- **7432** – OR Gate
- **7404** – NOT Gate (used twice)
- **7408** – AND Gate

### Procedure for EWB IC Setup:

#### Setup 1 (LHS): $(A + B)'$

1. Placed **7432 OR Gate IC** on the trainer board.
2. Connected A and B to two inputs of the OR gate.
3. Output was routed to a **NOT gate** using 7404 IC.
4. Final output connected to an LED.

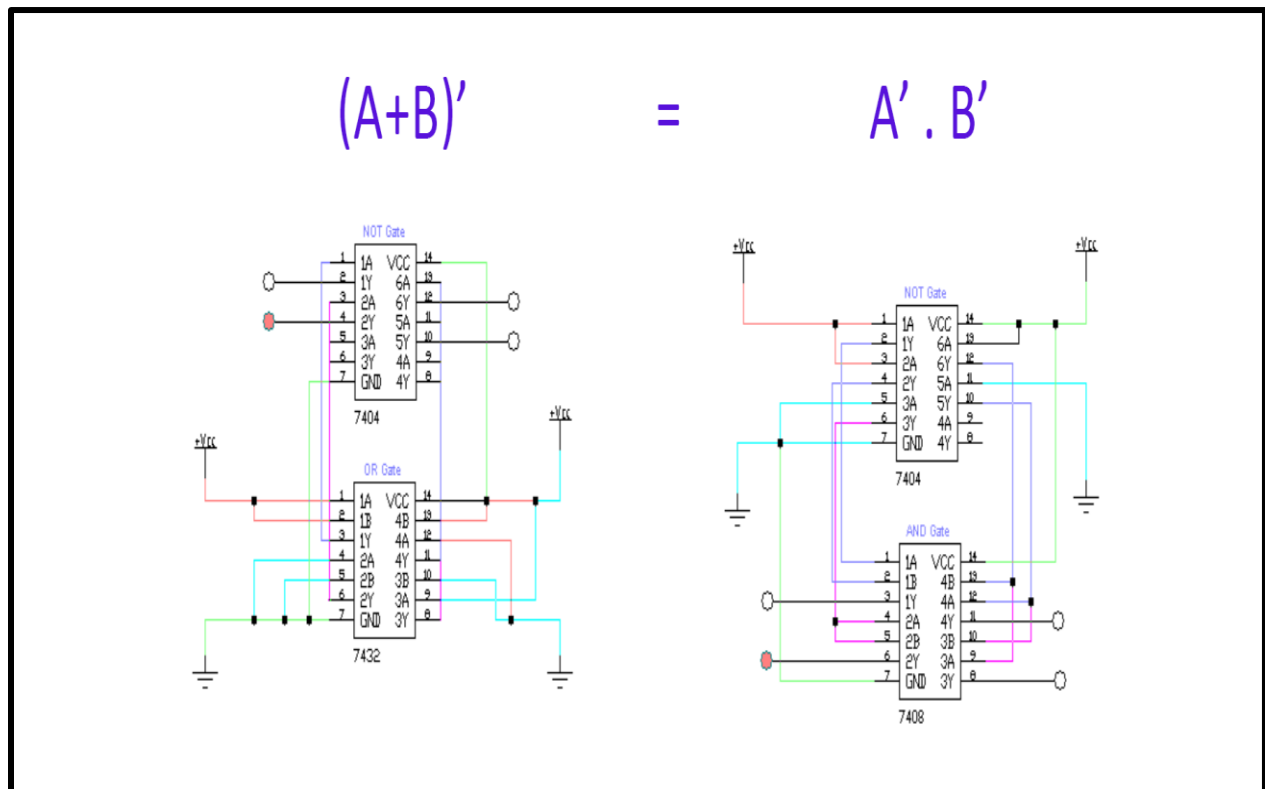


Figure 4: Proof Through IC Circuit

#### Setup 2 (RHS): $A' \cdot B'$

1. Input A sent through one NOT gate, input B through another.



2. Outputs from both NOTs connected to **7408 AND Gate IC**.
3. Final AND output connected to an **LED**.
4. Four LEDs used for testing four combinations (00, 01, 10, 11).

### TRUTH TABLE: $(A+B)' = A' \cdot B'$

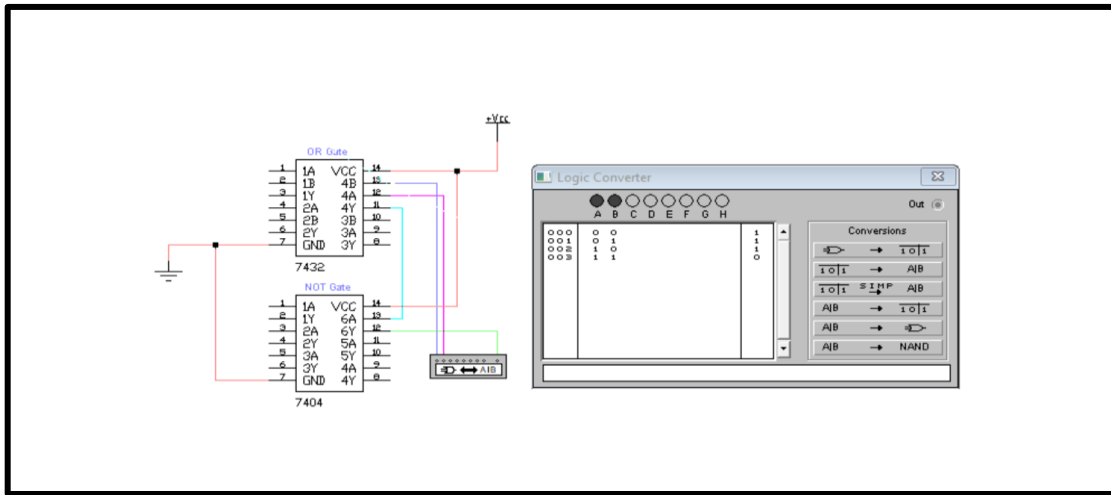


Figure 5: Truth Table through Logic Converter

A	B	A + B	$(A + B)'$	A'	B'	$A' \cdot B'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

### Result:

- For all combinations of A and B:
  - The output of LHS and RHS circuits **were identical**.

**De Morgan's Second Law was verified successfully** both practically and in simulation.