



**The University of Azad Jammu & Kashmir, Muzaffarabad**

## **Computer Architecture & Logic Design**

### **Lab 07: Encoder & Decoder**

**Student Name:**

**Shahzad Ahmed Awan**

**Roll No:**

**2024-SE-15**

**Course Title:**

**C&LD**

**Course Code:**

**CS-1206**

**Instructor:**

**Mam Sidra Rafique**

**Submission Date:**

**20-August-2025**

**Department of Software Engineering**

## LAB Objective

To design, simulate, and verify the working of:

1. A **Digital Encoder**
2. A **Digital Decoder**

using the Virtual Workbench tool, along with truth tables, circuit diagrams, and proper input-output verification.

### IMPORTANCE IN DIGITAL SYSTEMS

- **Data Conversion:** Encoders and decoders enable transformation between human-readable values and machine-level binary codes.
- **Control Signal Generation:** Essential in processors, memory addressing, multiplexing, and display systems.
- **Foundational Circuits:** Base building blocks for ALUs, I/O modules, communication systems, and instruction decoding.

## Encoder

### What is an Encoder?

An encoder is a combinational logic circuit that converts active input signals into a coded binary output. It has  $2^n$  input lines and n output lines, where only one input line is active at a time.


### Logic Equations:

For an 8-to-3 encoder:


- $A_2 = D_4 + D_5 + D_6 + D_7$
- $A_1 = D_2 + D_3 + D_6 + D_7$
- $A_0 = D_1 + D_3 + D_5 + D_7$

Only one input should be HIGH at any time for correct encoding.

### Block Diagram:

 

## Implementations in EWB

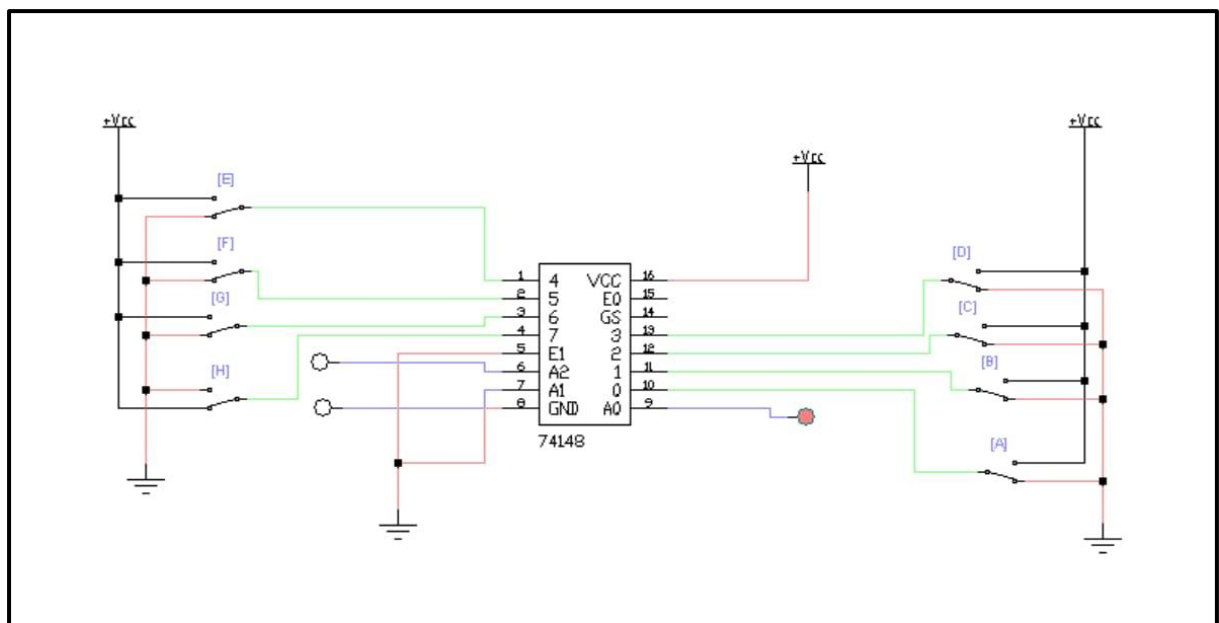

### TRUTH TABLE OF ENCODER (8 to 3)

[illegible]

## 2. Decoder

A Decoder is a combinational circuit that translates *n-bit binary input* into *2<sup>n</sup> unique outputs*. Each output represents one possible input combination and is activated when that binary code is received.

### Logic Equations

For a 3-to-8 decoder:

$$Y_0 = \bar{A}_2 \cdot \bar{A}_1 \cdot \bar{A}_0$$

$$Y_1 = \bar{A}_2 \cdot \bar{A}_1 \cdot A_0$$

$$Y_2 = \bar{A}_2 \cdot A_1 \cdot \bar{A}_0$$

$$Y_3 = \bar{A}_2 \cdot A_1 \cdot A_0$$


$$Y_4 = A_2 \cdot \bar{A}_1 \cdot \bar{A}_0$$

$$Y_5 = A_2 \cdot \bar{A}_1 \cdot A_0$$


$$Y_6 = A_2 \cdot A_1 \cdot \bar{A}_0$$

$$Y_7 = A_2 \cdot A_1 \cdot A_0$$


### Block Diagram:

 

## Implementation in EWB

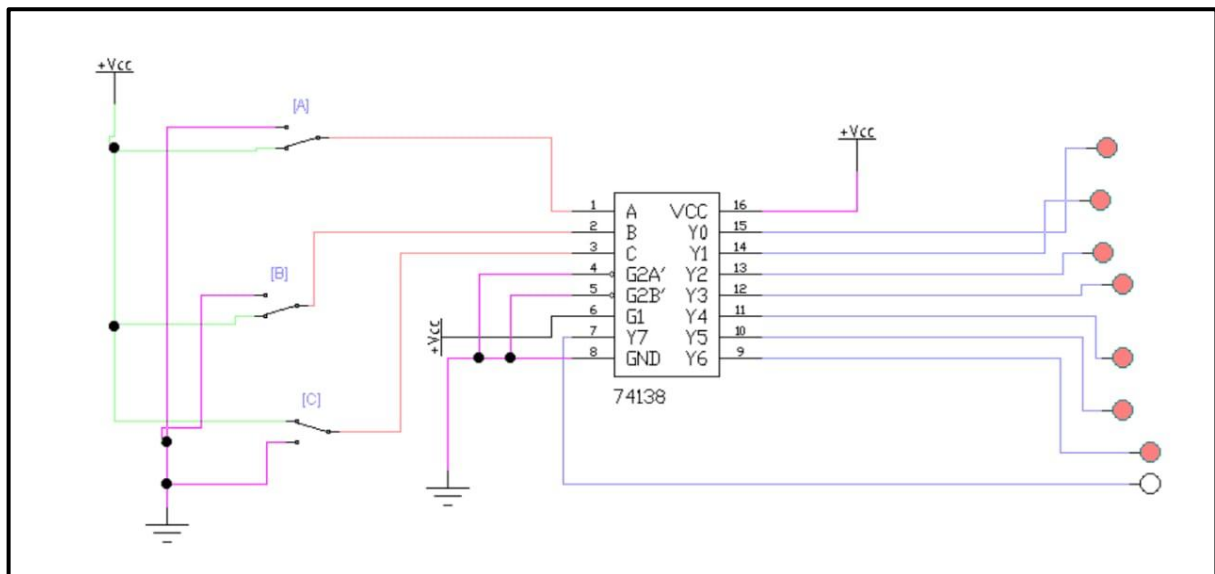

## Basic Gate Diagram

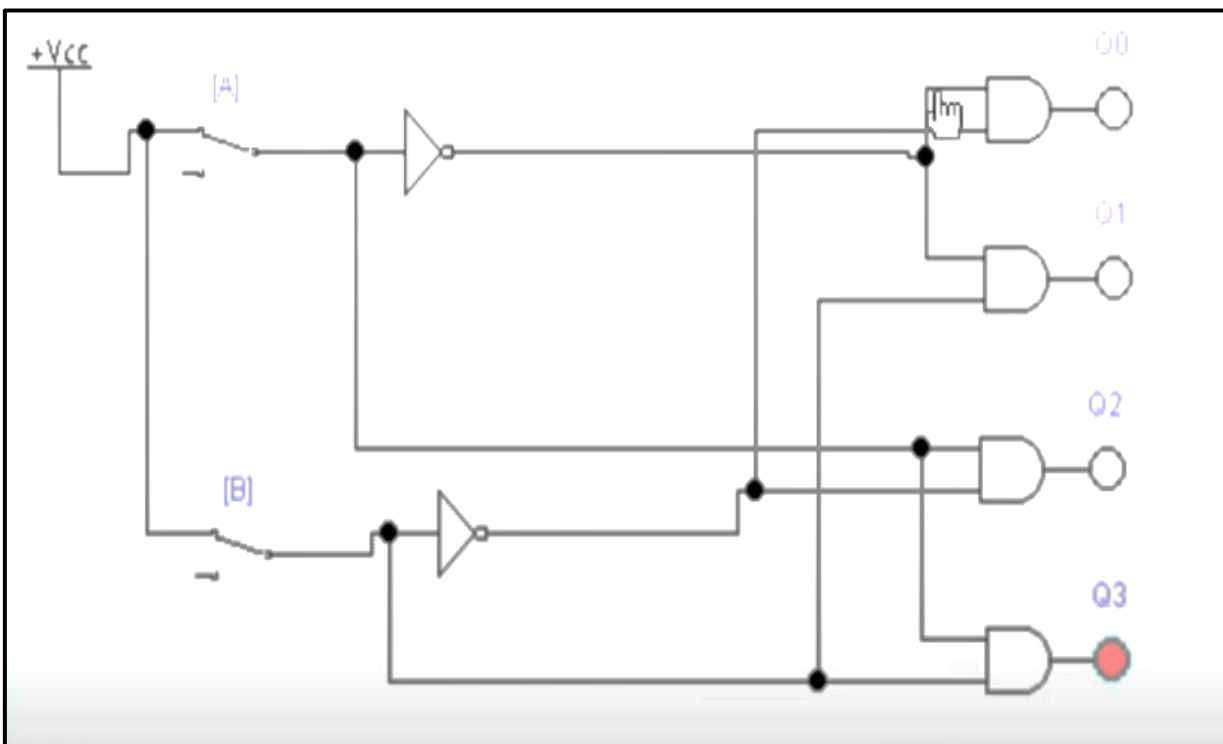

**TRUTH TABLE OF Decoder (3 to 8)**

A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0